

# EE140/240A Problem Set 7

sashank@berkeley.edu

Due: Mar 18, 2024

For all the problems in this homework, assume  $\mu_n C_{ox} = 0.5\text{mA/V}^2$ ,  $V_{Tn} = 0.3\text{V}$ , for the NMOS transistors, assume  $\mu_p C_{ox} = 0.4\text{mA/V}^2$ ,  $V_{Tp} = 0.4\text{V}$ , for the PMOS transistors. Also, assume that the channel length modulation parameter  $\lambda = 0$ , unless otherwise mentioned. Numbers adjacent to the MOS transistors indicate the  $(W/L)$  ratio of the transistors.

**Problem 1. 5+3 points** In lecture, we analyzed the large-signal behavior of a differential pair. In this question, you will re-derive the same. Please write your answers symbolically in terms of  $V_{DD}$ ,  $R_1$ ,  $I_0$ ,  $V_{CM}$ ,  $V_d$  and  $\mu_n C_{ox}$ ,  $\frac{W}{L}$  and  $V_{Tn}$ . Assume both  $M_1$  and  $M_2$  have the same  $\frac{W}{L}$ . Also, assume that  $V_{DD}$  is high enough that neither of  $M_1, M_2$  goes into triode.

 


Figure 1: Problem 1

- (a) Compute and plot  $v_{op}$  and  $v_{on}$  as a function of  $V_d$ .
- (b) Compute and mark the input voltage  $V_d$  for which the transistors  $M_1$  and  $M_2$  go into cut-off. What are the corresponding  $v_{op}$  and  $v_{on}$  values when  $M_1$  and  $M_2$  go into cut-off.

**Problem 2. (3+3+2)+(4+4+2)+(4+4+2)+(4+4+2) points** For each of the circuits shown below, evaluate the following: i) Differential mode gain  $A_{dm} = (v_{op} - v_{on})/v_d$ , ii) Common-mode gain  $A_{cm} = v_{op}/v_{cm}, v_{on}/v_{cm}$ , iii) Common mode rejection ratio (CMRR). Write your answers symbolically in terms of incremental parameters of the transistors  $g_m$  and  $r_o$  and resistor values, if any. Assume all transistors are in saturation. Other assumptions to be made for each circuit are stated below.

 


Figure 2: Problem 2(a)

- (a) Evaluate  $A_{dm}$ ,  $A_{cm}$  and CMRR for the circuit shown in Fig. 2. Consider channel length modulation for  $M_0$  alone and neglect it for the other transistors. Assume  $M_1, M_2$  have the same size and  $M_3, M_4$  have the same size.
- (b) Evaluate  $A_{dm}$ ,  $A_{cm}$  and CMRR for the circuit shown in Fig. 3. Consider channel length modulation for  $M_0$  alone and neglect it for the other transistors. Assume  $M_1, M_2$  have the same size and  $M_3, M_4$  have the same size.

 


Figure 3: Problem 2(b)

 


Figure 4: Problem 2(c)

- (c) Evaluate  $A_{dm}$ ,  $A_{cm}$  and CMRR for the circuit shown in Fig. 4. Consider channel length modulation for all transistors. Assume  $M_1, M_2$  have the same size and  $M_3 - M_6$  have the same size.
- (d) Evaluate  $A_{dm}$ ,  $A_{cm}$  and CMRR for the circuit shown in Fig. 5. Consider channel length modulation for  $M_0$  alone and neglect it for the other transistors. Assume  $M_1, M_2$  have the same size and  $M_3, M_4$  have the same size.

**Problem 3.  $(4+2+4+4)+(4+2+4+4)+(4+2+4+4)$  points** For all parts of this problem, assume  $V_{DD} = 1.8\text{V}$ ,  $V_B = 0.9\text{V}$ ,  $V_{B1} = 0.5\text{V}$ . Also, assume

 


Figure 5: Problem 2(d)

$$\lambda_n = \lambda_p = 0.2/V.$$

 


Figure 6: 1-stage op-amp without source follower

- (a) For the circuit in Fig. 6, compute the differential mode gain  $A_{dm} = v_{op}/v_d$ , common-mode gain  $A_{cm} = v_{op}/v_{cm}$ , the common-mode rejection ratio (CMRR) and the output resistance looking from  $v_{op}$ .
- (b) Now, the circuit in Fig. 6 is used as an op-amp and configured in unity gain feedback as shown in Fig. 7. Which terminal of the circuit in Fig. 6 is the positive terminal and which is the negative terminal of the op-amp?

 


Figure 7: Problem 3: Unity gain opamp

- (c) Now, assume  $R_L = \infty$ . Compute the gain  $v_{out}/v_{in}$  of the circuit in Fig. 6 configured in unity gain feedback. Also, compute the output resistance, and compare it with the output resistance without feedback.
- (d) Now, assume  $R_L = 100\Omega$ . Compute the gain  $v_{out}/v_{in}$  of the circuit in Fig. 6 configured in unity gain feedback. Comment on what you observe.
- (e) Now, we add a source follower to the circuit in Fig. 6 to get the circuit in Fig. 8. Compute the differential mode gain  $A_{dm} = v_{op}/v_d$  and the output resistance looking from  $v_{op}$ .
- (f) The circuit in Fig. 8 is used as an op-amp and configured in unity gain feedback as shown in Fig. 7. Which terminal of the circuit in Fig. 8 is the positive terminal and which is the negative terminal of the op-amp?
- (g) Now, assume  $R_L = \infty$ . Compute the gain  $v_{out}/v_{in}$  of the circuit in Fig. 8 configured in unity gain feedback. Also, compute the output

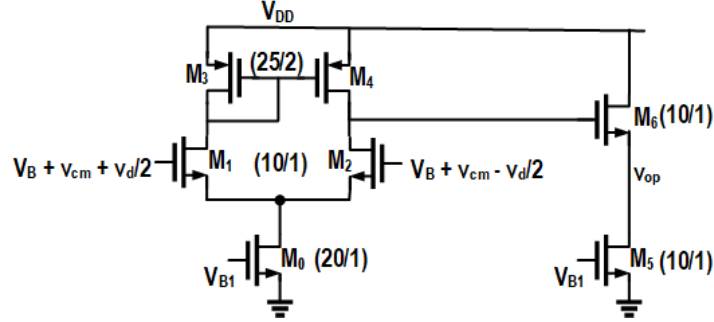


Figure 8: 1-stage op-amp with source follower

resistance, and compare it with the output resistance without feedback.

- (h) Now, assume  $R_L = 100\Omega$ . Compute the gain  $v_{out}/v_{in}$  of the circuit in Fig. 8 configured in unity gain feedback. Compare this with the answer obtained in part (d), and give your reasoning.

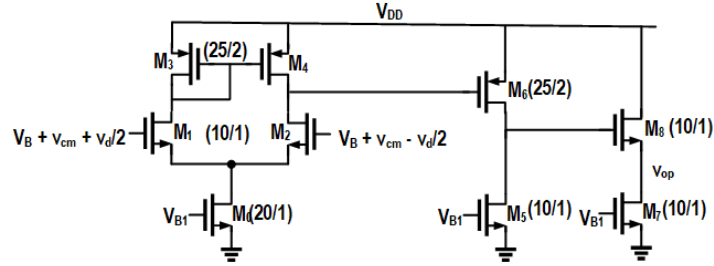


Figure 9: 2-stage op-amp with source follower

- (i) Now, we add another gain stage before the source follower to get a two-stage op-amp of Fig. 9. Compute the differential mode gain  $A_{dm} = v_{op}/v_d$  and the output resistance looking from  $v_{op}$ .
- (j) The circuit in Fig. 9 is used as an op-amp and configured in unity gain feedback as shown in Fig. 7. Which terminal of the circuit in Fig. 9 is the positive terminal and which is the negative terminal of the op-amp?
- (k) Now, assume  $R_L = \infty$ . Compute the gain  $v_{out}/v_{in}$  of the circuit in Fig. 9 configured in unity gain feedback. Also, compute the output resistance, and compare it with the output resistance without feedback.

- (l) Now, assume  $R_L = 100\Omega$ . Compute the gain  $v_{out}/v_{in}$  of the circuit in Fig. 9 configured in unity gain feedback. Compare this with the answers obtained in part (d) and (h), and give your reasoning.