

EE140/240A Problem Set 9

sashank@berkeley.edu

Due: Apr 18, 2024

For all the problems in this homework, assume $\mu_n C_{ox} = 0.5\text{mA/V}^2$, $V_{Tn} = 0.3\text{V}$, for the NMOS transistors, assume $\mu_p C_{ox} = 0.4\text{mA/V}^2$, $V_{Tp} = 0.4\text{V}$, for the PMOS transistors. Also, assume that the channel length modulation parameter $\lambda = 0$, unless otherwise mentioned. Numbers adjacent to the MOS transistors indicate the (W/L) ratio of the transistors.

Problem 1. 4+4+2 points Consider the amplifier shown below, which is very similar to the problem 2 in HW8. Assume $V_{DD} = 2\text{V}$, $V_B = 1\text{V}$, $V_{B1} = 0.5\text{V}$. Also, assume that $C_E = 0.2\text{pF}$. Assume $\lambda = \frac{0.2}{V}$.

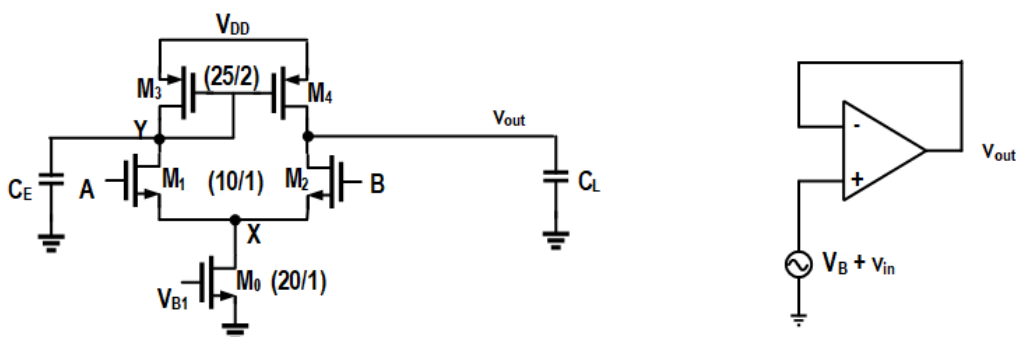


Figure 1: Problem 1

- For $C_L = 1\text{pF}$, compute the unity gain frequency and phase margin when the op-amp is connected in unity gain feedback.
- For $C_L = 10\text{pF}$, compute the unity gain frequency and phase margin when the op-amp is connected in unity gain feedback. Compare this with the previous part.

- (c) For $C_L = 10\text{pF}$, what is the maximum slew rate for a rising and falling input step?

Problem 2. 4+4+4+4 points Consider the 2-stage amplifier shown below. Assume $V_{DD} = 2\text{V}$, $V_B = 1\text{V}$, $V_{B1} = 0.5\text{V}$. Also, assume that $C_C = 10\text{pF}$. Assume $\lambda = \frac{0.2}{\text{V}}$.

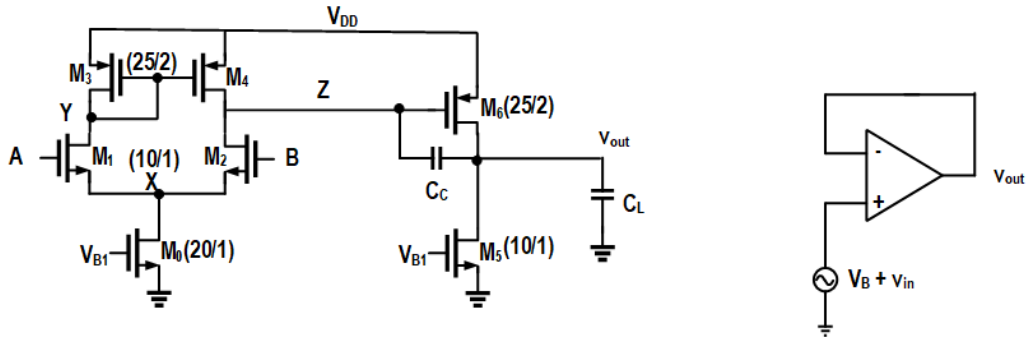


Figure 2: Problem 2

- (a) For $C_L = 1\text{pF}$, compute the unity gain frequency and phase margin when the op-amp is connected in unity gain feedback.
- (b) For $C_L = 10\text{pF}$, what is the maximum slew rate for a rising and falling input step?
- (c) For $C_L = 10\text{pF}$, compute the unity gain frequency and phase margin when the op-amp is connected in unity gain feedback. Compare this with part (a). What comment can you make about the effect of the load capacitance C_L in a 1-stage op-amp and a 2-stage op-amp?
- (d) For $C_L = 10\text{pF}$, what is the maximum slew rate for a rising and falling input step?

Problem 3. 4+6+2 points Consider the telescopic cascode op-amp shown below. Assume $V_{DD} = 2\text{V}$, $V_{B1} = 0.4\text{V}$, $V_{B2} = 1\text{V}$. Also, assume that $C_L = 10\text{pF}$.

- (a) Assume that the op-amp is connected in unity gain feedback, and is provided a sinusoidal input of the form $A\sin(\omega_0 t)$. What should be the

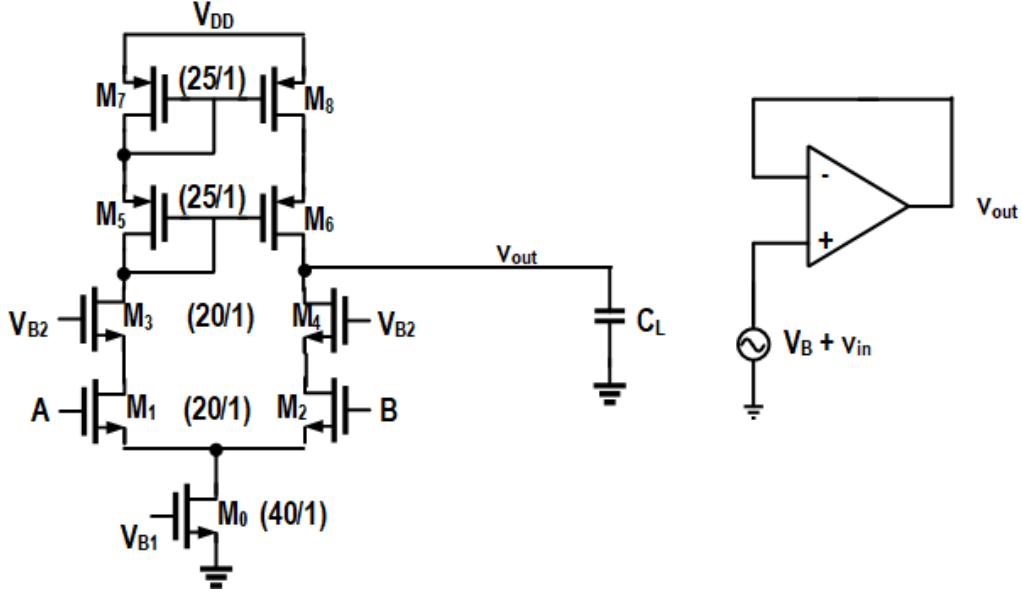


Figure 3: Problem 3

input bias V_B to maximize the output swing? What is the maximum output swing A thus obtained? You may assume $\lambda = 0$ for this part to simplify your calculations.

- (b) Find the open-loop differential gain of the op-amp. Use the value of V_B obtained in part (a) as the input bias voltage of transistors M_1, M_2 . Assume $\lambda = \frac{0.2}{V}$.
- (c) What is the maximum slew rate for a rising and falling input step?

Problem 4. 6+4+3+8 points

Consider the folded cascode op-amp shown below. Assume $V_{DD} = 2V$, $V_{B1} = 0.4V$, $V_{B2} = 1.5V$. Also, assume that $C_L = 10pF$.

- (a) Assume that the op-amp is connected in unity gain feedback, and is provided a sinusoidal input of the form $A\sin(\omega_0 t)$. What should be the input bias V_B and the bias voltage V_{B1} to maximize the output swing? What is the maximum output swing A thus obtained? You may assume $\lambda = 0$ for this part to simplify your calculations.
- (b) What is the maximum slew rate for a rising and falling input step?

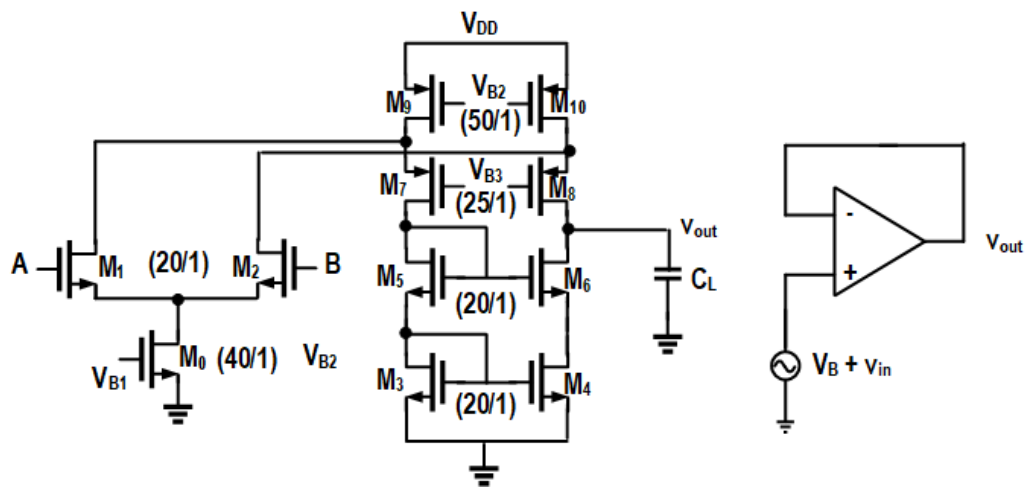


Figure 4: Problem 4

- (c) Find the open-loop differential gain of the op-amp. Use the value of V_B obtained in part (a) as the input bias voltage of transistors M_1, M_2 , and V_{B1} as the bias voltage for transistors M_7, M_8 . Assume $\lambda = \frac{0.2}{V}$.
- (d) Now, assume that the sizes of M_9, M_{10} are increased to (125/1). Repeat parts (a) and (b) with the new transistor sizes and compare against parts (a) and (b).